

Shift Register Expansion Of XMOS XS1 Devices

REV 1.0

2011/05/11
XMOS © 2011, All Rights Reserved.



1 Introduction

This document provides useful information on using shift registers to expand the I/O capabilities of XMOS XS1 devices.

XMOS XS1 devices have a large array of I/O capabilities, but in certain applications more (fairly low-speed) I/O ports are required than are available on the device. Although it is possible to step up to a larger XS1 device with either more xCORE Tiles or more pins, this is not always possible or desirable due to cost constraints. Situations where this is likely include driving arrays of LEDs or reading arrays of buttons.

A solution to this issue is to use shift registers to serialize or deserialize the input or output respectively. This means a few pins on the XS1 device can be used to connect to potentially hundreds of inputs or outputs at relatively low cost.


For further details about individual XS1 devices refer to the relevant device datasheet.

2 Shift Registers For Input

To capture input from multiple pins and send it into an XS1 device, a parallel in / serial out shift register can be used. Typically these are 8-bits long, such as the 74HC165, which is available from a variety of manufacturers and costs \$0.085 in low volume (1000 off quantity from Digi-Key).

Then device has the following signals:

- ▶ *DATA_IN* (*DS* or *SI*) - the serial data input to the shift register.
- ▶ *SCLK* (*CP* or *CK*) - the serial clock to clock the data through the shift register.
- ▶ *CE_N* (\overline{CE} or *CK_INH*) - the chip enable (active low) signal.
- ▶ *PL_N* (\overline{PL} or *S/L*) - loads the contents of the input register into the shift register.
- ▶ *DATA_OUT* (*DATA_OUT* or *QH*) - the data output from the shift register.
- ▶ *DATA_OUT_N* ($\overline{DATA_OUT}$ or \overline{QH}) - the inverted data output from the shift register.
- ▶ *D[7:0]* - the 8-bits of parallel data input.

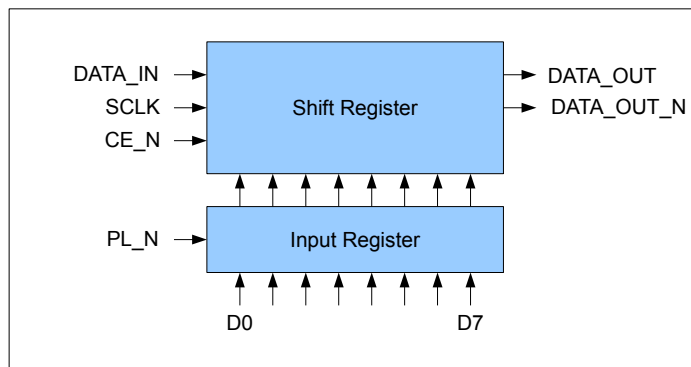


The diagram above details the internal structure of a parallel in / serial out shift register. It can be seen that there is an input register, which on the rising edge of *PL_N* latches the values of *D[7:0]* into the shift register. The shift register then serially shifts the data out of *DATA_OUT*, one bit at a time, on each clock input rising edge. At the same time data is shifted from *DATA_IN* into the register. This allows multiple devices to be chained together to form one long shift register. The *CE_N* enables the shift register to commence shifting, allowing the interface pins to be shared with another interface.

3 Shift Registers For Output

To output data to multiple pins using an XS1 device a serial in / parallel out shift register is used. Typically these are 8bits long such as the 74HC595, which is available from a variety of manufacturers and costs \$0.086 in low volume (1000 off quantity from Digi-Key).

Then device has the following signals:

- ▶ *DATA_IN* (*DS* or *SER*) - the serial data input to the shift register.
- ▶ *SCLK* (*SH_CP* or *SCK*) - the serial clock to clock the data through the shift register.
- ▶ *MR_N* (\overline{MR} or \overline{SCLR}) - master reset to wipe the output of the device.
- ▶ *LATCH* (*ST_CP* or *RCK*) - latches the contents of the shift register into the storage register.
- ▶ *OE_N* (\overline{OE} or \overline{G}) - enable the output to the pins, otherwise the pins are tri-stated.
- ▶ *DATA_OUT* (*Q7'*) - the data output from the shift register to chain multiple devices together.
- ▶ *Q[7 : 0]* - the 8-bits of parallel data output.

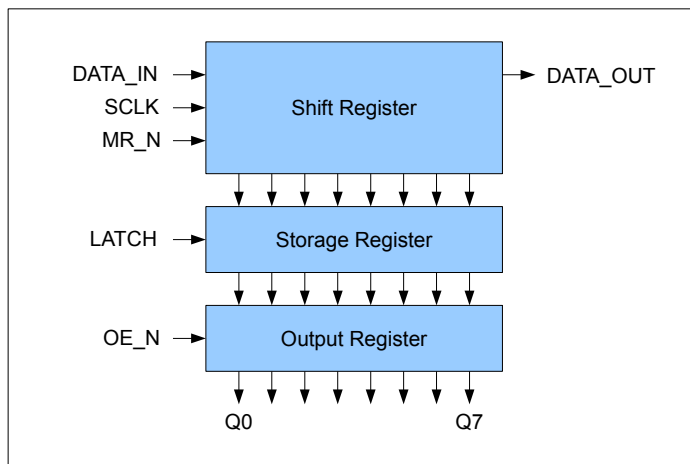


The diagram above details the internal structure of a serial in / parallel out shift register. The shift register shifts the data in from *DATA_IN*, one bit at a time, on each clock input rising edge. At the same time the data currently in the shift register gets shifted out of *DATA_OUT*. This allows multiple devices to be chained together to form one long shift register. The *MR_N* is the master reset signal, which resets all of the shift registers. On the rising edge of the *LATCH* signal the contents of the shift register are latched from the shift register into the output register. When *OE_N* (active low) is low, the output register is enabled and the data is available on *Q[7 : 0]*. Otherwise, when *OE_N* is high, the output pins are tri-stated into a high impedance state.

4 Example Shift Register Board


To demonstrate the use of shift registers for both input and output, a board has been designed that uses 4 x 1-bit ports to interface to 2 shift registers. One is for input and one is for output, connected to 8 surface-mount push-button switches and 8 LEDs respectively.

 The board is designed to plug onto an I/O expansion bank on an XK-1/XK-1A or XCard format board. It gets 3V3 power and ground from the board which it is plugged into.



The next section provides detailed schematics for this board.

 5 Schematics For Example Shift Register Board



6 Software For Example Shift Register Board

Example software to loop the button input back out to the LEDs on the board is shown below. It is written in XC and consists of two threads. One thread simply reflects any data sent to (to loop the buttons back to the LEDs) and the other interfaces to the buttons and LEDs.

There are many different ways of writing the interface code in XC. This one has been designed to use only one timer and plain input and output operations. Such scheme is useful in typical applications, where some or all of the signals are parts of multi-bit ports (and serialization or port conditions cannot be used). This is because it may have to be put into a constrained application where there are not many resources available.

```

1 #include <xs1.h>
2 #include <platform.h>
3 #include <print.h>
4 #include <stdlib.h>
5
6 // Ports for the serial shift registers
7 on stdcore[0]: out port p_latch = XS1_PORT_1A;
8 on stdcore[0]: out port p_clk = XS1_PORT_1B;
9 on stdcore[0]: out port p_mosi = XS1_PORT_1C;
10 on stdcore[0]: in port p_miso = XS1_PORT_1D;
11
12 // Run the clock at 1MHz (2 x 0.5us delays (50 reference clock tick))
13 #define DELAY 50
14
15 // Thread to reflect the data send to it, to loop back the threads and buttons.
16 void test_reflector ( chanend c_leds, chanend c_buttons )
17 {
18     char my_data;
19
20     // Loop forever
21     while ( 1 )
22     {
23         // Get the value for the buttons
24         c_buttons :> my_data;
25
26         // Send it out to the LEDs
27         c_leds <: my_data;
28     }
29 }
30
31 // Test thread to interface with LEDs and buttons
32 void test_leds_buttons ( chanend c_leds, chanend c_buttons )
33 {
34     char led_val = 0, button_val, tmp_but;
35     unsigned int i, time, loop_time;
36     timer t;
37
38     // Get the initial timer value
39     t := loop_time;
40
41     // Setup the initial output values
42     p_latch <: 1;
43     p_clk <: 0;
44     p_mosi <: 0;
45
46     // Loop forever
47     while ( 1 )
48     {
49         select
50         {
51             // Receive a new value for the LEDs over a channel
52             case c_leds :> led_val:
53                 break;
54         }

```

```

55 // At 100Hz sample the buttons and output the value to the LEDs
56 case t when timerafter(loop_time + 100000) => loop_time:
57
58 // Copy over the loop_time value, so the timing can use it
59 time = loop_time;
60
61 // Initialize the button value.
62 button_val = 0;
63
64 // Place a rising edge on the latch signal
65 // This clocks the previously loaded LED data out and captures the button data
66 p_latch <= 0;
67 t when timerafter(time + DELAY) => time;
68 p_latch <= 1;
69 t when timerafter(time + DELAY) => time;
70
71 // Cycle through 8 bits
72 for ( i = 0; i < 8; i++ )
73 {
74 // Output the data, MSB bit first.
75 p_mosi <= (char) (led_val >> i);
76
77 // Wait for half a bit time
78 t when timerafter(time + DELAY) => time;
79
80 // Set the clock high
81 p_clk <= 1;
82
83 // Get the current bit from the shift register
84 p_miso := tmp_but;
85
86 // Add the bit to the button value, LSB bit first.
87 button_val = button_val + (tmp_but << i);
88
89 // Wait for half a bit time
90 t when timerafter(time + DELAY) => time;
91
92 // Set the clock low
93 p_clk <= 0;
94 }
95
96 // Send the button value out
97 c_buttons <= button_val;
98
99 break;
100 }
101 }
102 }
103
104 // Program entry point
105 int main()
106 {
107 chan c_leds, c_buttons;
108
109 par
110 {
111 // XCore 0
112 on stdcore[0] : test_reflector( c_leds, c_buttons );
113 on stdcore[0] : test_leds_buttons( c_leds, c_buttons );
114 }
115
116 return 0;
117 }

```

 

7 XA-USBA-LED Add-On Board

An add-on board had been designed which uses the general purpose input/output expansion header (J19) on the XS1-L2 USB audio board (XR-USB-AUDIO-2.0-MC) to demonstrate the interface to 6 LED bars for level meters. The boards are design to be chained - seven linked together perform satisfactorily. This makes a total length of 42 x LED bars, each being driven by an 8-bit 74VHC595 shift register, making a total shift register length of 336 bits.


To demonstrate the interfacing using a single 4-bit port rather than 1-bit ports, all of the signals are connected to a single 4-bit port with the signal mappings below.


- ▶ 4F0 = *SER_IN*
- ▶ 4F1 = *CLK*
- ▶ 4F2 = *RCK*
- ▶ 4F3 = *OE_N*

Very High Speed CMOS (VHC) series devices are used to allow the writing of data very quickly to the LED bars, whilst minimizing processing time.



 The next section provides detailed schematics for this board.



 

X MOS

Copyright © 1997 X MOS Corp.

74HC164

XA-USB-A-LED

74HC164


LED_BAR

1V0


DATE


10/07/2010


1 OF 1

 

X MOS			
Copyright © 1997 X MOS Corp. All rights reserved.			
X MOS XS1 NAME			
XA-USB-A-LED			
REV	REV NAME	REV	REV
A3	LED_BAR	1V0	1V0
DATE	DATE	REV	REV
	1997.07.20	1	1

 

 

 

9 Software For XA-USBA-LED Add-On Board

Example software for a chain of seven XA-USBA-LED add-on boards is shown below. It is written in XC and consists of a single thread, lighting each column on in the chain in turn. The software takes account of the fact that the shift register on each board is effectively byte-reversed relative to the chaining of the boards.

```

1 // Includes
2 #include <xs1.h>
3 #include <platform.h>
4 #include <print.h>
5 #include <stdlib.h>
6
7
8 // Ports for the serial shift registers
9 on stdcore[1]: out port p_led = XS1_PORT_4F;
10 on stdcore[1]: clock my_clk = XS1_CLKBLK_1;
11
12 // 0 = SER_IN
13 // 1 = CLK
14 // 2 = RCK
15 // 3 = OE_N
16
17
18 // Defines for the LED panels
19 #define NUM_PANELS 7
20 #define NUM_COLUMNS_PER_PANEL 6
21 #define TOTAL_COLUMNS (NUM_PANELS * NUM_COLUMNS_PER_PANEL)
22
23
24 // Test thread to interface with LEDs
25 void test_leds ( void )
26 {
27     char led_val[TOTAL_COLUMNS], temp = 0;
28     signed int panel, column, row;
29     unsigned int i, loop_time, my_row = 0;
30     timer t;
31
32     // Configure the output to run from a clk blk at 25MHz clock rate
33     set_clock_div(my_clk,2);
34     configure_out_port(p_led,my_clk,0);
35     start_clock(my_clk);
36
37     // Get the initial timer value
38     t := loop_time;
39
40     // Setup the initial output values
41     p_led <: 0;
42
43     // Wipe the led_vals
44     for ( i = 0; i < TOTAL_COLUMNS; i++ )
45     {
46         led_val[i] = 0x00;
47     }
48
49     // Loop forever
50     while ( 1 )
51     {
52         select
53         {
54             // At 10Hz update and output the value to the LEDs
55             case t when timerafter(loop_time + 10000000) := loop_time:
56
57                 // Loop though all the panels (boards)
58                 for ( panel = 0; panel < NUM_PANELS; panel++ )
59                 {
60                     // Loop through the 6 columns
61                     for ( column = 5; column > -1; column-- )
62                     {
63                         // Loop through each row of the column of 8 bits
64                         for ( row = 7; row > -1; row-- )

```

```
65         {
66             // Get the required bit of the LED data, MSB bit first.
67             temp = (led_val[(panel * 6) + column] >> row) & 0x1;
68
69             // Place the data onto the port and set the clock high
70             p_led <: (temp + 2);
71
72             // Set the clock low
73             p_led <: temp;
74         }
75     }
76 }
77
78 // Clock the data into the output registers
79 p_led <: 4;
80
81 // Set the current row to 0
82 led_val[my_row++] = 0x00;
83
84 // Prevent my_row from overflowing out of led_val
85 if (my_row == TOTAL_COLUMNS)
86 {
87     my_row = 0;
88 }
89
90 // Set the next row to 1
91 led_val[my_row] = 0xFF;
92
93 break;
94 }
95 }
96 }
97
98 // Program entry point
99 int main()
100 {
101     {
102         par
103         {
104             // XCore 1
105             on stdcore[1] : test_leds( );
106         }
107     }
108     return 0;
109 }
```

10 Related Documents

Information about XMOS technology is primarily available from the XMOS web site; please see <http://xmos.com/documentation> for the latest documents or click on one of the links below to find out more information.

Document title	Document reference
Programming XC on XMOS Devices	programming-xc-xmos-devices
XK-1 Hardware Manual	xk-1-hardware-manual
USB-AUDIO-2.0-MC Hardware Manual	usb-audio-20-mc-hardware-manual
NXP 74HC165 Datasheet	74hc165-datasheet
NXP 74HC595 Datasheet	74hc595-datasheet

Document History

Date	Release	Comment
2011-05-11	1.0	First release



Copyright © 2011, All Rights Reserved.

Xmos Ltd. is the owner or licensee of this design, code, or Information (collectively, the "Information") and is providing it to you "AS IS" with no warranty of any kind, express or implied and shall have no liability in relation to its use. Xmos Ltd. makes no representation that the Information, or any particular implementation thereof, is or will be free from any claims of infringement and again, shall have no liability in relation to any such claims.

XMOS and the XMOS logo are registered trademarks of Xmos Ltd. in the United Kingdom and other countries, and may not be used without written permission. All other trademarks are property of their respective owners. Where those designations appear in this book, and XMOS was aware of a trademark claim, the designations have been printed with initial capital letters or in all capitals.